

Appendix I: Ohm's Law

Example 1. Two long coaxial metal cylinders (radii a and b) are separated by material of conductivity σ . If they are maintained at a potential difference V , what current flows from one to the other, in a length L ?

First we need to determine the Field. Using Gauss' Theorem,

$$\oint \mathbf{E} = \frac{Q_{\text{enc}}}{\epsilon_0}$$
$$E 2\pi s L = \frac{\lambda L}{\epsilon_0}$$

thus

$$\mathbf{E} = \frac{\lambda}{2\pi s \epsilon_0} \hat{\mathbf{s}}$$

While current is


$$I = \int \mathbf{J} \cdot d\mathbf{a} = \int \sigma \mathbf{E} \cdot d\mathbf{a} = \frac{\sigma}{\epsilon_0} \lambda L$$

and the potential difference between the cylinders is

$$V(a) - V(b) = V = - \int_b^a \mathbf{E} \cdot d\mathbf{l} = \frac{\lambda}{2\pi \epsilon_0} \ln \frac{b}{a}$$

so

$$I = \frac{2\pi \sigma L}{\ln b/a} V$$

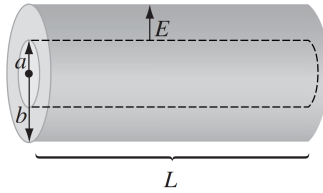

Appendix II: Circuits

Impedance. For resistor, impedance, or rather resistance, is defined by Ohm's Law (derivated)

$$R = \frac{V}{I}$$

We define capacitive reactance as:

$$X_C = -i \frac{1}{2\pi f C}$$

The inductive reactance can be found using:

$$X_L = i 2\pi f L$$

Resonance. This phenomenon occurs when our circuit has maximum value of current, which resulted from having minimum impedance. Since minimum impedance occur when $X_L = X_C$,

$$f = \frac{1}{2\pi\sqrt{LC}}$$

RC Circuits. Applying Kirchhoff's loop rule to the circuit after the switch is thrown to position a , we get

$$\begin{aligned} iR + \frac{1}{C}q &= \varepsilon \\ \dot{q} + \frac{1}{RC}q &= \frac{\varepsilon}{R} \end{aligned}$$

this is first order ODE, which can be easily solved using integral factor

$$I = \int \frac{1}{RC} dt = \frac{t}{RC}$$

Then

$$\begin{aligned} q &= e^{-t/RC} \int \frac{\varepsilon}{R} e^{t/RC} dt + A e^{-t/RC} \\ q &= C\varepsilon + A e^{-t/RC} \end{aligned}$$

Applying boundary condition $q(0) = 0$, we get $A = -C\varepsilon$, thus

$$q = C\varepsilon(1 - e^{-t/RC})$$

Since $i = dq/dt$

$$i = \frac{\varepsilon}{R} e^{-t/RC}$$

Time constant $\tau \equiv RC$ of the circuit represents the time interval during which the current decreases to $1/e$ of its initial value. Now, imagine that the capacitor is completely charged. If the switch is now thrown to position b , the capacitor begins to discharge through the resistor. The differential equation becomes

$$\dot{q} + \frac{1}{RC}q = 0$$

with general solution

$$q = A e^{-t/RC}$$

Applying boundary condition $q(0) = Q_i$, we get $A = Q_i$, thus

$$q = Q_i e^{-t/RC}$$

As for the instantaneous current

$$i = -\frac{Q_i}{RC} e^{-t/RC} = -I_i e^{-t/RC}$$

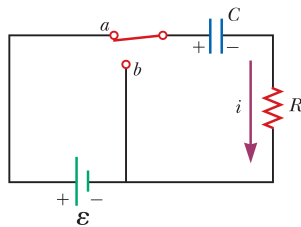


Figure: RC Circuit

RL Circuits. Let's apply Kirchhoff's loop rule to the circuit when S_2 is set to a and switch S_1 is closed

$$L\dot{i} + iR = \varepsilon$$

$$\dot{i} + i\frac{R}{L} = \frac{\varepsilon}{L}$$

As before, I use integral factor

$$I = \int \frac{R}{L} dt = \frac{R}{L}t$$

Then

$$i = e^{-Rt/L} \int \frac{\varepsilon}{L} e^{Rt/L} dt + Ae^{-Rt/L}$$

$$i = \frac{\varepsilon}{L} + Ae^{-Rt/L}$$

Applying boundary condition $i(0) = 0$, we get $A = -\varepsilon/R$, thus

$$i = \frac{\varepsilon}{R}(1 - e^{-Rt/L})$$

Since $q = \int i dt$

$$q = \frac{\varepsilon}{R}(1 - \frac{L}{R}e^{-Rt/L})$$

Now, suppose S_2 is thrown from a to b. The differential equation becomes

$$\dot{i} + i\frac{R}{L} = 0$$

with general solution

$$i = Ae^{-Rt/L}$$

Applying boundary condition $i(0) = I_i$, we get $A = I_i$, thus

$$i = I_i e^{-Rt/L}$$

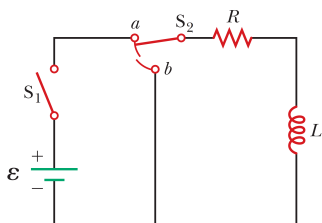


Figure: RL Circuit

RLC Circuits. If the applied voltage varies sinusoidally with time

$$v = V_m \sin \omega t$$

then current in the circuit is given by

$$i = I_m \sin \omega t - \phi$$

where

$$\phi = \arctan^{-1} \frac{Z_{im}}{Z_{Re}}$$

is some phase angle between the current and the applied voltage.