

## Appendix I: Ohm's Law

### Example 1.

Two long coaxial metal cylinders (radii  $a$  and  $b$ ) are separated by material of conductivity  $\sigma$ . If they are maintained at a potential difference  $V$ , what current flows from one to the other, in a length  $L$ ?

First we need to determine the Field. Using Gauss' Theorem,

$$\oint \mathbf{E} = \frac{Q_{\text{enc}}}{\epsilon_0}$$
$$E 2\pi s L = \frac{\lambda L}{\epsilon_0}$$

thus

$$\mathbf{E} = \frac{\lambda}{2\pi s \epsilon_0} \hat{\mathbf{s}}$$

While current is


$$I = \int \mathbf{J} \cdot d\mathbf{a} = \int \sigma \mathbf{E} \cdot d\mathbf{a} = \frac{\sigma}{\epsilon_0} \lambda L$$

and the potential difference between the cylinders is

$$V(a) - V(b) = V = - \int_b^a \mathbf{E} \cdot d\mathbf{l} = \frac{\lambda}{2\pi \epsilon_0} \ln \frac{b}{a}$$

so

$$I = \frac{2\pi \sigma L}{\ln b/a} V$$

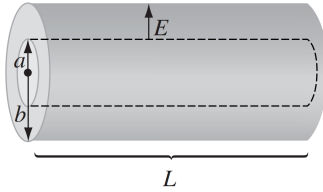

## Appendix II: Circuits

**Impedance.** For resistor, impedance, or rather resistance, is defined by Ohm's Law (derivated)

$$R = \frac{V}{I}$$

We define capacitive reactance as:

$$X_C = -i \frac{1}{2\pi f C}$$

The inductive reactance can be found using:

$$X_L = i 2\pi f L$$

**Resonance.** This phenomenon occurs when our circuit has maximum value of current, which resulted from having minimum impedance. Since minimum impedance occur when  $X_L = X_C$ ,

$$f = \frac{1}{2\pi\sqrt{LC}}$$

**RC Circuits.** Applying Kirchhoff's loop rule to the circuit after the switch is thrown to position  $a$ , we get

$$\begin{aligned} iR + \frac{1}{C}q &= \varepsilon \\ \dot{q} + \frac{1}{RC}q &= \frac{\varepsilon}{R} \end{aligned}$$

this is first order ODE, which can be easily solved using integral factor

$$I = \int \frac{1}{RC} dt = \frac{t}{RC}$$

Then

$$\begin{aligned} q &= e^{-t/RC} \int \frac{\varepsilon}{R} e^{t/RC} dt + A e^{-t/RC} \\ q &= C\varepsilon + A e^{-t/RC} \end{aligned}$$

Applying boundary condition  $q(0) = 0$ , we get  $A = -C\varepsilon$ , thus

$$q = C\varepsilon(1 - e^{-t/RC})$$

Since  $i = dq/dt$

$$i = \frac{\varepsilon}{R} e^{-t/RC}$$

Time constant  $\tau \equiv RC$  of the circuit represents the time interval during which the current decreases to  $1/e$  of its initial value. Now, imagine that the capacitor is completely charged. If the switch is now thrown to position  $b$ , the capacitor begins to discharge through the resistor. The differential equation becomes

$$\dot{q} + \frac{1}{RC}q = 0$$

with general solution

$$q = A e^{-t/RC}$$

Applying boundary condition  $q(0) = Q_i$ , we get  $A = Q_i$ , thus

$$q = Q_i e^{-t/RC}$$

As for the instantaneous current

$$i = -\frac{Q_i}{RC} e^{-t/RC} = -I_i e^{-t/RC}$$

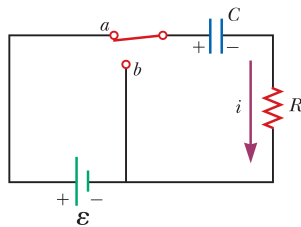


Figure: RC Circuit

**RL Circuits.** Let's apply Kirchhoff's loop rule to the circuit when  $S_2$  is set to a and switch  $S_1$  is closed

$$L\dot{i} + iR = \varepsilon$$

$$\dot{i} + i\frac{R}{L} = \frac{\varepsilon}{L}$$

As before, I use integral factor

$$I = \int \frac{R}{L} dt = \frac{R}{L}t$$

Then

$$i = e^{-Rt/L} \int \frac{\varepsilon}{L} e^{Rt/L} dt + Ae^{-Rt/L}$$

$$i = \frac{\varepsilon}{L} + Ae^{-Rt/L}$$

Applying boundary condition  $i(0) = 0$ , we get  $A = -\varepsilon/R$ , thus

$$i = \frac{\varepsilon}{R}(1 - e^{-Rt/L})$$

Since  $q = \int i dt$

$$q = \frac{\varepsilon}{R}(1 - \frac{L}{R}e^{-Rt/L})$$

Now, suppose  $S_2$  is thrown from a to b. The differential equation becomes

$$\dot{i} + i\frac{R}{L} = 0$$

with general solution

$$i = Ae^{-Rt/L}$$

Applying boundary condition  $i(0) = I_i$ , we get  $A = I_i$ , thus

$$i = I_i e^{-Rt/L}$$

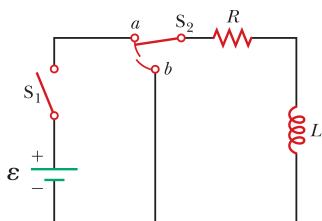


Figure: RL Circuit

**RLC Circuits.** If the applied voltage varies sinusoidally with time

$$v = V_m \sin \omega t$$

then current in the circuit is given by

$$i = I_m \sin \omega t - \phi$$

where

$$\phi = \arctan^{-1} \frac{Z_{im}}{Z_{Re}}$$

is some phase angle between the current and the applied voltage.